 


Help

At 2:17 of the video, Professor Albonesi says "NAND gates," but he meant to say "AND gates."

MEMORY



	4:17 / 4:17	1.0x			
--	-------------	------	--	--	--

Now a multi-bit latch or a register, which is a set of flip-flops, those are one dimensional structures in that they can store only a single piece of data. With the memory, we have a two dimensional structure that can store multiple pieces of data. Now we can think of this as a k by m array of stored bits. Now we need an address to pick which location in our memory we're going to read or write. Now if we have n address bits then that gives us two to the n locations. In our example, we're saying that's k. Now the address space is the number of locations in our memory, which is usually a power of two, because we're dealing with binary numbers for our address. In this case, we have k locations. And the addressability is the number of bits that we store in every location. And in this case, that's m bits. Here's an example of a four by three memory. Here we have four locations and each one of those stores three bits. Now this has a lot of pieces to it, but these are all pieces that we've already covered in the course. Let's first start with each of the locations, each cell in the memory, which is where we store a bit.

04/14/2015 10:17 AM

In this example, in this type of memory that

we're going to talk about,

we have in each cell a D latch.

So you should recognize this as a D latch.

Here's the write enable and here's the D input to our D latch.

And each one of these locations, each one of these 12 locations,

here is identical.

We have a D latch.

Now we have a column of data that feeds into each location.

So in this case, we have 3 bits in every location.

So you see that we feed in a data bit into each of the columns.

We have the same data bit going to each of the four cells in each column.

Now we need to be able to select one of these rows.

We're going to select one row of three bits in this memory.

And the way we do that is by using our address.

So because we have four rows, we need two address bits

to identify the row that we want to read or write.

And the way we do that is with these NAND gates and these bubbles.

Now you should recognize this as a two to four decoder.

Remember, with a two to four decoder, we have two inputs

and we have four outputs, and one of those outputs is a one

and the other are zero.

So this allows us to select one and only one row with our address bits.

Now the outputs of the decoder are used to pick one of these rows.

Now let's look at the data output of the top row.

So when our address is zero, zero, then the output of the top decoder

will be a one, and we're going to have a one

at the input of each of those AND gates for the data coming out.

So what's that going to do?

That's going to allow the data that's out of each of those cells

to pass through their NAND gates in order to go to the output.

Now what's going to happen to the other NAND gates

in the rows that aren't selected?

The bottom three decoder outputs will be zero.

And so the remaining nine AND gates for the data output will be zero

are going to be zero.

So what's that going to do?

That's going to allow our data from the first row

to appear at the output queue.

Now let's talk about how we write the first row.

We need to have again our address be zero,
zero in order

to be able to select those top three cells.

But now our write enable input is going to be a
one.

Previously when we read, we had that be a zero
so that we didn't overwrite anything in those
cells.

With the write enable being a one and the
output of the decoder being a one,

then we will have the write enable input for

Download transcript .txt


Help

Show Discussion

 New Post

1. CHECK YOUR UNDERSTANDING (1/1 point)

How many address bits are required for a memory with 64 locations, each of which holds 32 bits?

- ☐ 3
- ☐ 4
- ☐ 5
- ☒ 6 

EXPLANATION

With 64 locations, 6 bits are required since $2^6 = 64$, or $\log_2 64 = 6$. The number of bits in each location is irrelevant.

Final Check

Save

Hide Answer

You have used 1 of 2 submissions

Show Discussion

 New Post

Help

A 4×4 memory array contains the following data:

0001

0010

0100

1000

The inputs are as follows: $D3D2D1D0 = 1100$, $A1A0 = 10$, $WE = 0$. What action will occur?

- ☐ The value 1100 will be written into the second memory location.
- ☐ The value 1100 will be written into the third memory location.
- ☒ The value 0100 will appear at the output. ✓
- ☐ No action will be taken.

EXPLANATION

Since $WE = 0$, a read operation will be performed. The address 10 points to the third location. Therefore, the value 0100 will be read out of that location.

Final Check

Save

Hide Answer

You have used 1 of 2 submissions

Show Discussion

 New Post



EdX offers interactive online classes and MOOCs from the world's best universities. Online courses from MITx, HarvardX, BerkeleyX, UTx and many other universities. Topics include biology, business, chemistry, computer science, economics, finance, electronics, engineering, food and nutrition, history, humanities, law, literature, math, medicine, music, philosophy, physics, science, statistics and more. EdX is a non-profit online initiative created by founding partners Harvard and MIT.

© 2015 edX Inc.

EdX, Open edX, and the edX and Open edX logos are registered trademarks or trademarks of edX Inc.

04/14/2015 10:17 AM

