 


BASIC LOGIC GATES




	2:36 / 2:36	1.0x			
--	-------------	------	--	--	--






Download transcript

.txt

Show Discussion


 New Post

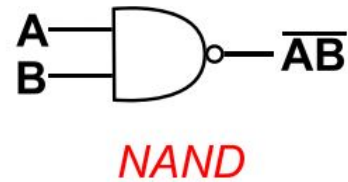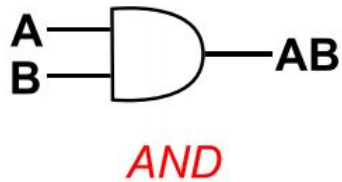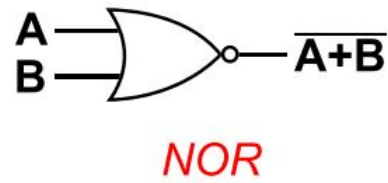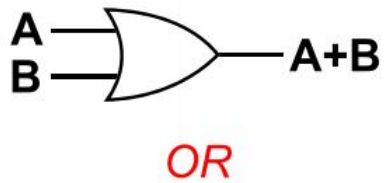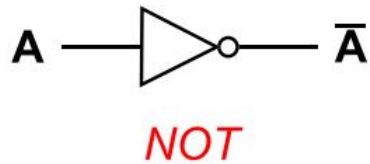Please click [here](#) to open the Basic Logic Gates Diagram in a new window. You can print it out by right-clicking on your mouse.



1. CHECK YOUR UNDERSTANDING

Consider the following CMOS circuit:

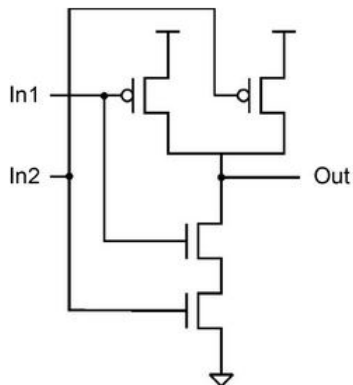

1 A. CHECK YOUR UNDERSTANDING (1/1 point)

Fill in the truth table values for Out. **You have only ONE submission.**

In1	In2	Out	
0	0	<input type="text" value="1"/>	Answer: 1
0	1	<input type="text" value="1"/>	Answer: 1
1	0	<input type="text" value="1"/>	Answer: 1
1	1	<input type="text" value="0"/>	Answer: 0

EXPLANATION

When either or both of the inputs are 0, a connection is made to the supply voltage and the connection to ground is broken, which makes the output a 1.

Only when both inputs are 1 is a connection made to ground and the connection to the supply voltage broken, which makes the output a 0.

[Hide Answer](#)*You have used 1 of 1 submissions*[Show Discussion](#)[New Post](#)**1 B. CHECK YOUR UNDERSTANDING** (1/1 point)

This circuit implements which of the following logic functions?

☐ AND☐ OR☒ NAND☐ NOR**EXPLANATION**

A NAND outputs a 0 when all inputs are 1 and a 1 otherwise.

[Final Check](#)[Save](#)[Hide Answer](#)*You have used 1 of 2 submissions*[Show Discussion](#)[New Post](#)

computer science, economics, finance, electronics, engineering, food and nutrition, history, humanities, law, life science, medicine, music, philosophy, physics, science, statistics and more. EdX is a non-profit online initiative created by founding partners Harvard and MIT.

© 2015 edX Inc.

EdX, Open edX, and the edX and Open edX logos are registered trademarks or trademarks of edX Inc.

Terms of Service and Honor Code

Privacy Policy (Revised 10/22/2014)



Contact

FAQ

edX Blog

Donate to edX

Jobs at edX



LinkedIn

<https://courses.edx.org/courses/CornellX/ENGRI1210x/1...>



Google+



Tumblr



Meetup



Reddit



Youtube

Help