


[Courseware](#) [Course Info](#) [Discussion](#) [Wiki](#) [Progress](#) [Discussion Guidelines](#) [Resources](#) [Exploring Engineering](#)

[Syllabus](#) [How to Use Jade](#)
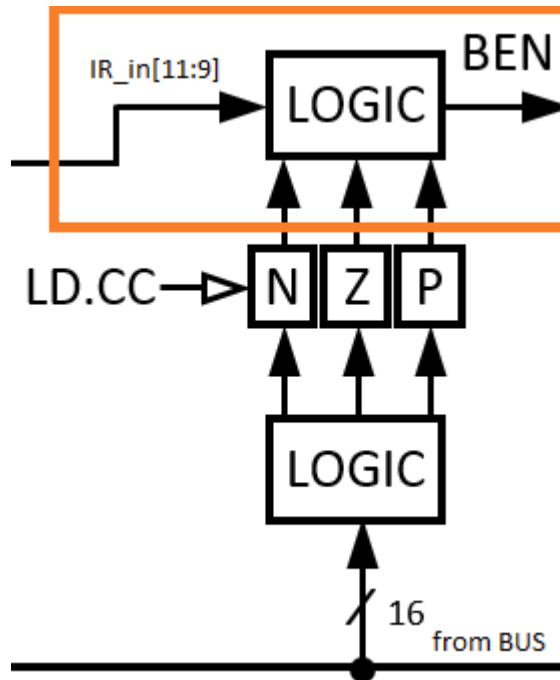
## Help

Design the LC-3 BEN logic, and test it using the provided test file.

The area of the LC-3 we are designing is shown here, in red:




The design takes as inputs IR[11:9] and the value of the 3-bit CC (condition codes: N, Z, P) register and generates a single BEN output.

Refer to the BR Instruction Unit video to design this logic.

**Save your design as a library component.**

Help

LC-3 LITE BRANCH ENABLE LOGIC (1/1 point)

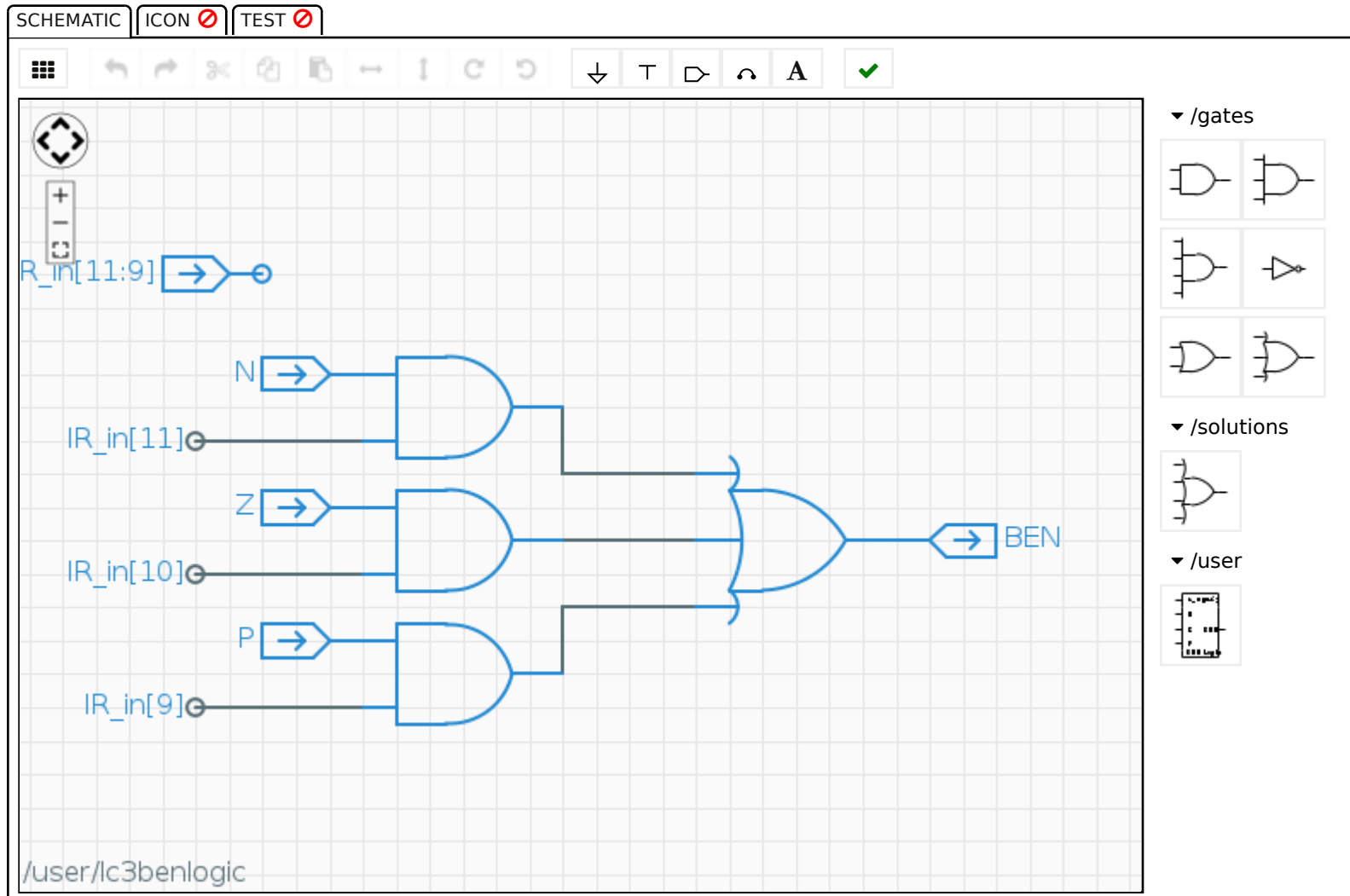Module:    

Click component to select, click and drag on background for area select, shift-click and drag on background to pan

[Jade 2.2.43 \(2015 © MIT EECS\)](#)

[Check](#)[Hide Answer](#)[Help](#)

EdX offers interactive online classes and MOOCs from the world's best universities. Online courses from MITx, HarvardX, BerkeleyX, UTx and many other universities. Topics include biology, business, chemistry, computer science, economics, finance, electronics, engineering, food and nutrition, history, humanities, law, literature, math, medicine, music, philosophy, physics, science, statistics and more. EdX is a non-profit online initiative created by founding partners Harvard and MIT.

© 2015 edX Inc.

EdX, Open edX, and the edX and Open edX logos are registered trademarks or trademarks of edX Inc.

[Terms of Service and Honor Code](#)

[Privacy Policy \(Revised 10/22/2014\)](#)

4 of 4



## About edX

[About](#)

[News](#)

[Contact](#)

[FAQ](#)

[edX Blog](#)

[Donate to edX](#)


[Jobs at edX](#)


## Follow Us


 [Facebook](#)

 [Twitter](#)


 [LinkedIn](#)

 [Google+](#)

 [Tumblr](#)

 [Meetup](#)

 [Reddit](#)

 [Youtube](#)