

LAB 6. 8-to-1 Multiplexer

We will be building another major component of our processor this week, the register file. There are 5 labs, an 8-to-1 mux, its 16-bit version, a loadable register with set and reset, a special 16-bit version, and finally the register file itself.

In this first lab, we will build a 1-bit 8-to-1 mux. When Select[2:0] is 000, A should be sent to Z, and so on. When Select[2:0] is 111, H should be sent to Z.


Design your 8-to-1 mux with the provided gates in the parts bin. You may use your `/user/or4` if you load it. There is also an `or4` in the parts bin.

The icon for this circuit, `/user/mux8to1`, appears in the parts bin. Don't use that or you'll get a "recursive inclusion of module" error!

Test it, save it, and submit it to edX via the check button. The next lab will be the 16-bit version.

8-TO-1 MULTIPLEXER (1/1 point)

Module: /user/mux8to1

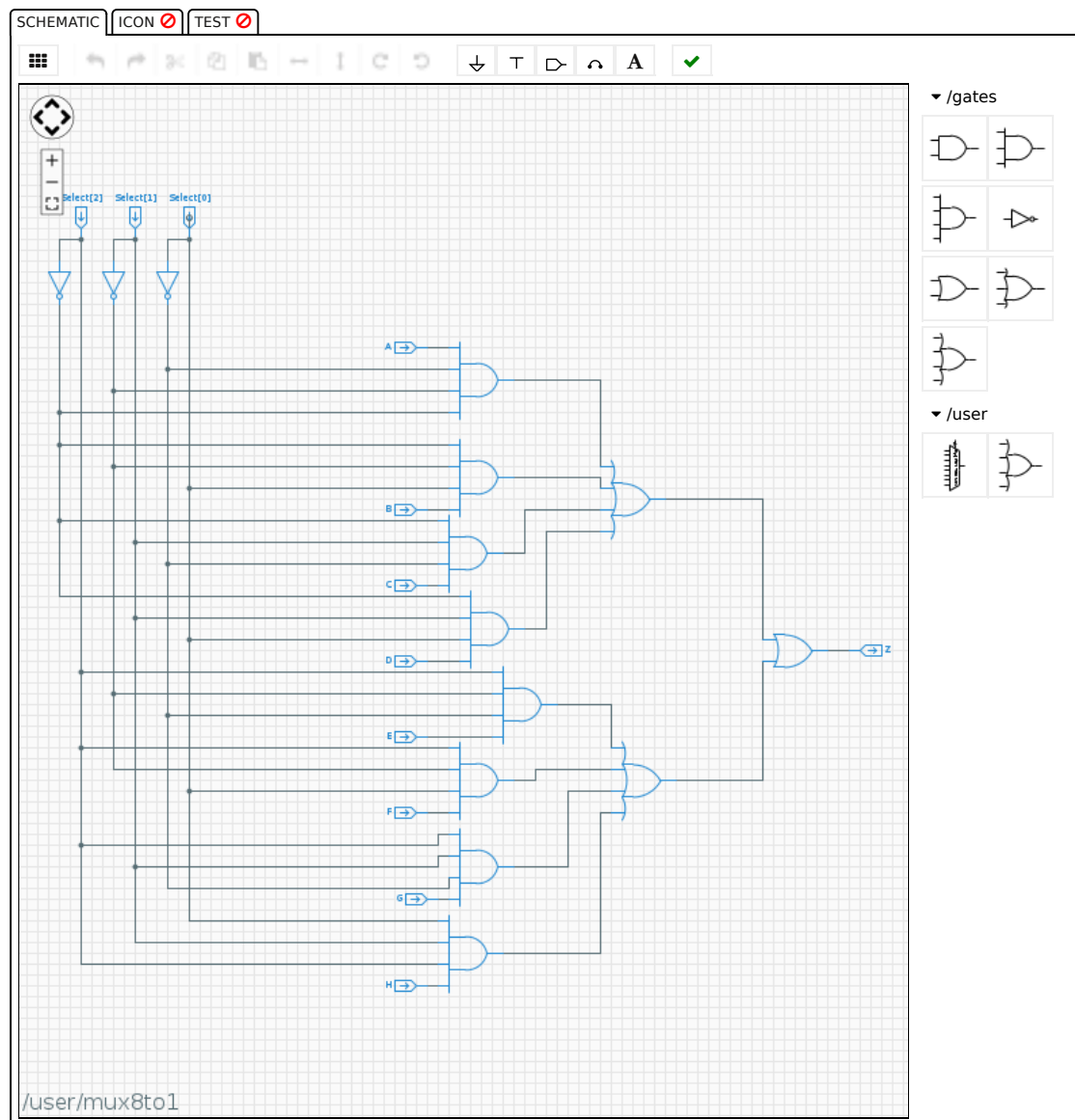[Jade 2.2.40 \(2015 © MIT EECS\)](#)


Check

Hide Answer

Show Discussion

New Post



 universities. Online courses from MITx, HarvardX, BerkeleyX, MITx and many other universities. Topics include biology, business, chemistry, computer science, economics, finance, electronics, engineering, food and nutrition, history, humanities, law, literature, math, medicine, music, philosophy, physics, science, statistics and more. EdX is a non-profit online initiative created by founding partners Harvard and MIT.

Help

© 2015 edX Inc.

EdX, Open edX, and the edX and Open edX logos are registered trademarks or trademarks of edX Inc.

[Terms of Service and Honor Code](#)

[Privacy Policy \(Revised 10/22/2014\)](#)



About edX

[About](#)

[News](#)

[Contact](#)

[FAQ](#)

[edX Blog](#)

[Donate to edX](#)

[Jobs at edX](#)

<https://courses.edx.org/courses/CornellX/ENGRI1210x/1...>


Follow Us

 [Facebook](#)

 [Twitter](#)


 [LinkedIn](#)

 [Google+](#)

 [Tumblr](#)

 [Meetup](#)

 [Reddit](#)

 [Youtube](#)