 


At 2:15, Professor Albonesi says that he has four OR gates. He meant to say:

"I have a four input OR gate..."

FULL ADDER



	4:51 / 4:51	1.0x			
--	-------------	------	--	--	--

Download transcript .txt

Show Discussion

New Post

1. CHECK YOUR UNDERSTANDING (1/1 point)

Which of the following is true about a Full Adder circuit? [Check all that apply]

- ☐ S and C<sub>out</sub> are never both 0.
- ☐ S and C<sub>out</sub> are never both 1.
- ☒ Whenever exactly one of A, B, and C<sub>in</sub> are 1, S = 1 and C<sub>out</sub> = 0. ✓
- ☒ Whenever exactly two of A, B, and C<sub>in</sub> are 1, S = 0 and C<sub>out</sub> = 1. ✓

## EXPLANATION

A	B	$C_{in}$	S	$C_{out}$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

The first two statements are false. In the first row,  $S = C_{out} = 0$ . In the last,  $S = C_{out} = 1$ . The last two statements are seen to be true by inspection of the truth table.

Hide Answer

You have used 2 of 2 submissions

Show Discussion

 New Post


edX offers interactive online classes and MOOCs from the world's best universities. Online courses from MITx, HarvardX, BerkeleyX, UTx and many other universities. Topics include biology, business, chemistry, computer science, economics, finance, electronics, engineering, food and nutrition, history, humanities, law, literature, math, medicine, music, philosophy, physics, science, statistics and more. EdX is a non-profit online initiative created by founding partners Harvard and MIT.

© 2015 edX Inc.

EdX, Open edX, and the edX and Open edX logos are registered trademarks or trademarks of edX Inc.

Terms of Service and Honor Code

Privacy Policy (Revised 10/22/2014)



## About edX

About

News

Contact

FAQ

edX Blog

Donate to edX

Jobs at edX


## Follow Us


 Facebook

 Twitter


 LinkedIn

 Google+

 Tumblr

 Meetup

 Reddit

 Youtube