
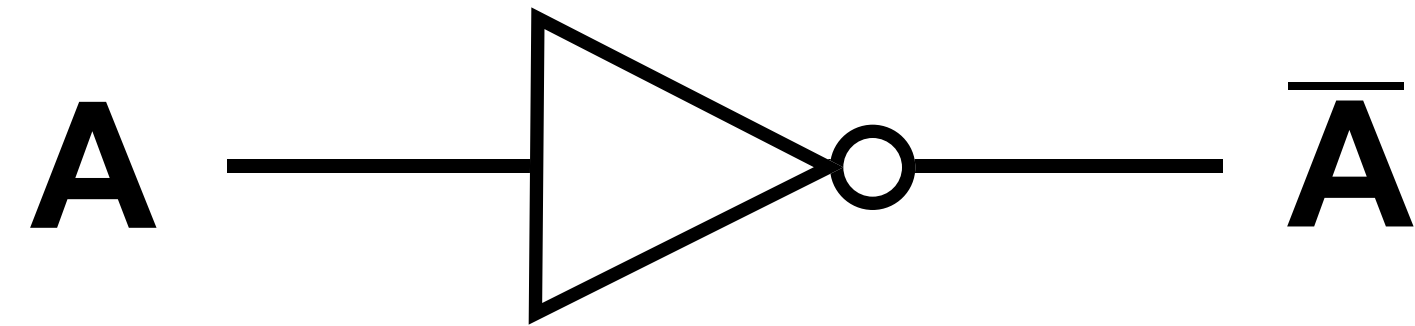



Basic Logic Gates

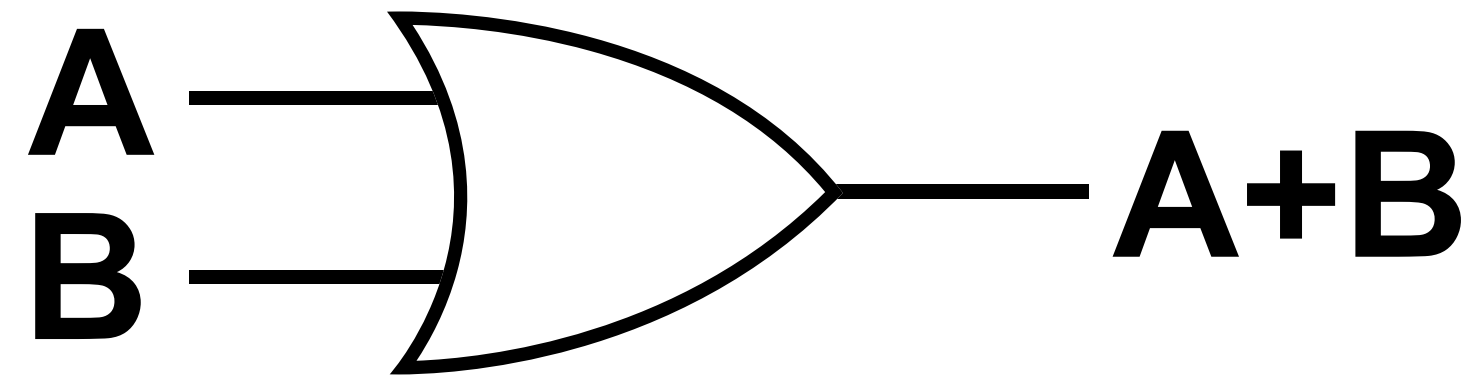


NOT




OR

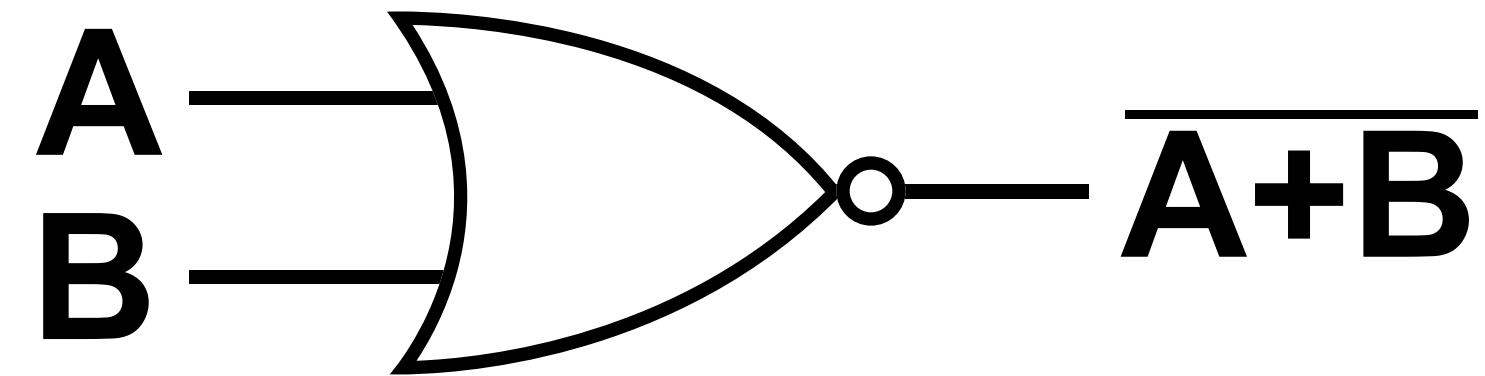

NOR

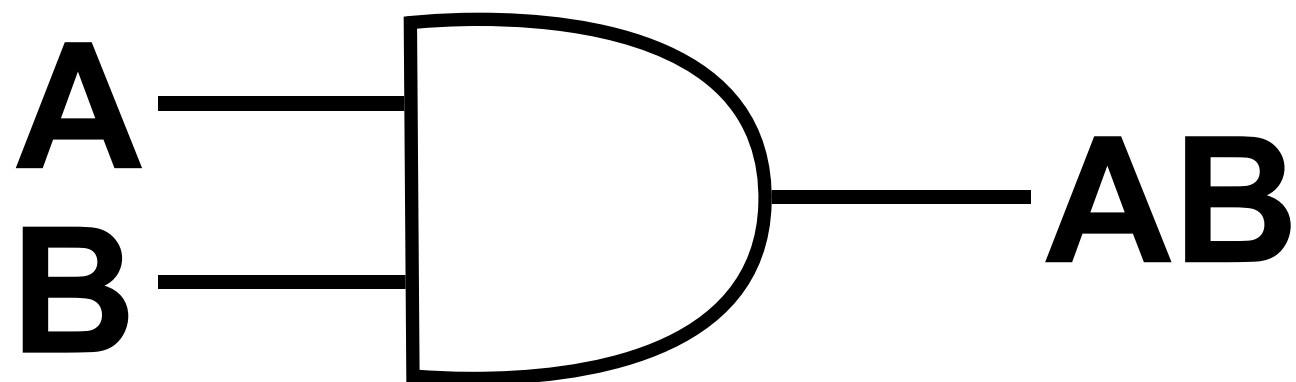

AND

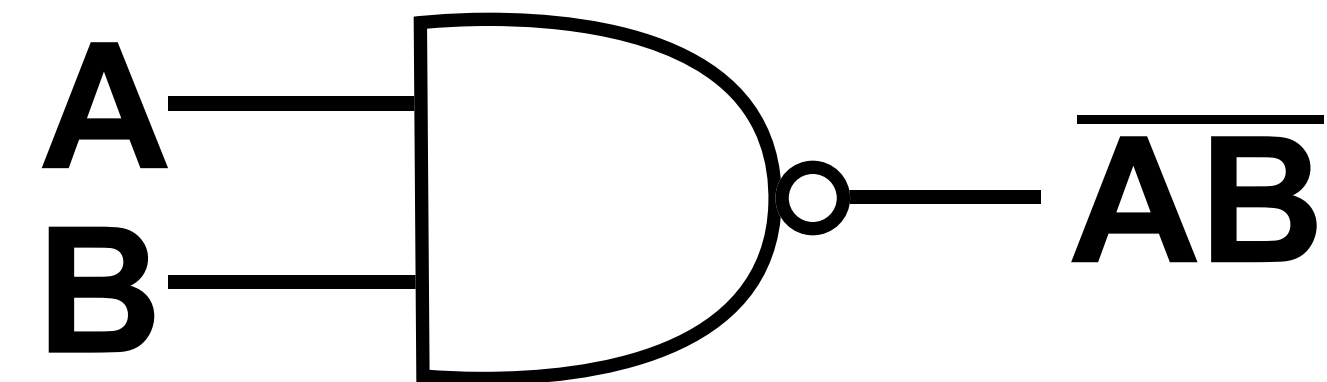

NAND