 


DEMORGAN'S LAW



6:21 / 6:21	1.0x			
-------------	------	--	--	--

Download transcript .txt

Show Discussion

New Post

1. CHECK YOUR UNDERSTANDING (1/1 point)

Which of the following is functionally equivalent to a NAND gate? [Check all that apply]

- ☒ An AND gate followed by a NOT gate. ✓
- ☒ A NAND gate followed by two back-to-back NOT gates. ✓
- ☒ A NOR gate with both the inputs and output inverted. ✓
- ☐ A NOR gate with just the inputs inverted.

EXPLANATION

1 of 2  
The first is equivalent since a NAND by definition is the inverse of AND.

04/02/2015 03:59 PM

Help

The third is equivalent since DeMorgan's Law equates a NAND with an OR with its inputs inverted, and a NOR with its output inverted is the same as an OR.

The fourth is not equivalent since it is like an OR with both inputs and output inverted, which is equivalent to AND, not NAND.

Hide Answer

*You have used 2 of 2 submissions*

Show Discussion

 New Post



EdX offers interactive online classes and MOOCs from the world's best universities. Online courses from MITx, HarvardX, BerkeleyX, UTx and many other universities. Topics include biology, business, chemistry, computer science, economics, finance, electronics, engineering, food and nutrition, history, humanities, law, literature, math, medicine, music, philosophy, physics, science, statistics and more. EdX is a non-profit online initiative created by founding partners Harvard and MIT.

© 2015 edX Inc.

EdX, Open edX, and the edX and Open edX logos are registered trademarks or trademarks of edX Inc.

[Terms of Service and Honor Code](#)

[Privacy Policy \(Revised 10/22/2014\)](#)



#### About edX

[About](#)

[News](#)

[Contact](#)

[FAQ](#)

[edX Blog](#)

[Donate to edX](#)

[Jobs at edX](#)


#### Follow Us


 [Facebook](#)


 [Twitter](#)


 [LinkedIn](#)

 [Google+](#)

 [Tumblr](#)

 [Meetup](#)

 [Reddit](#)

 [Youtube](#)