


LAB 1. MUXES AND DECODERS

Design, only using **NOT** and **AND** gates, a 3-to-8 decoder and test it using the provided test file. You should have only **three (3)** NOT and **eight (8)** AND gates in your design.

After testing and checking, save this as a library component.

3 TO 8 DECODER (1/1 point)

Module: /user/decode3to8

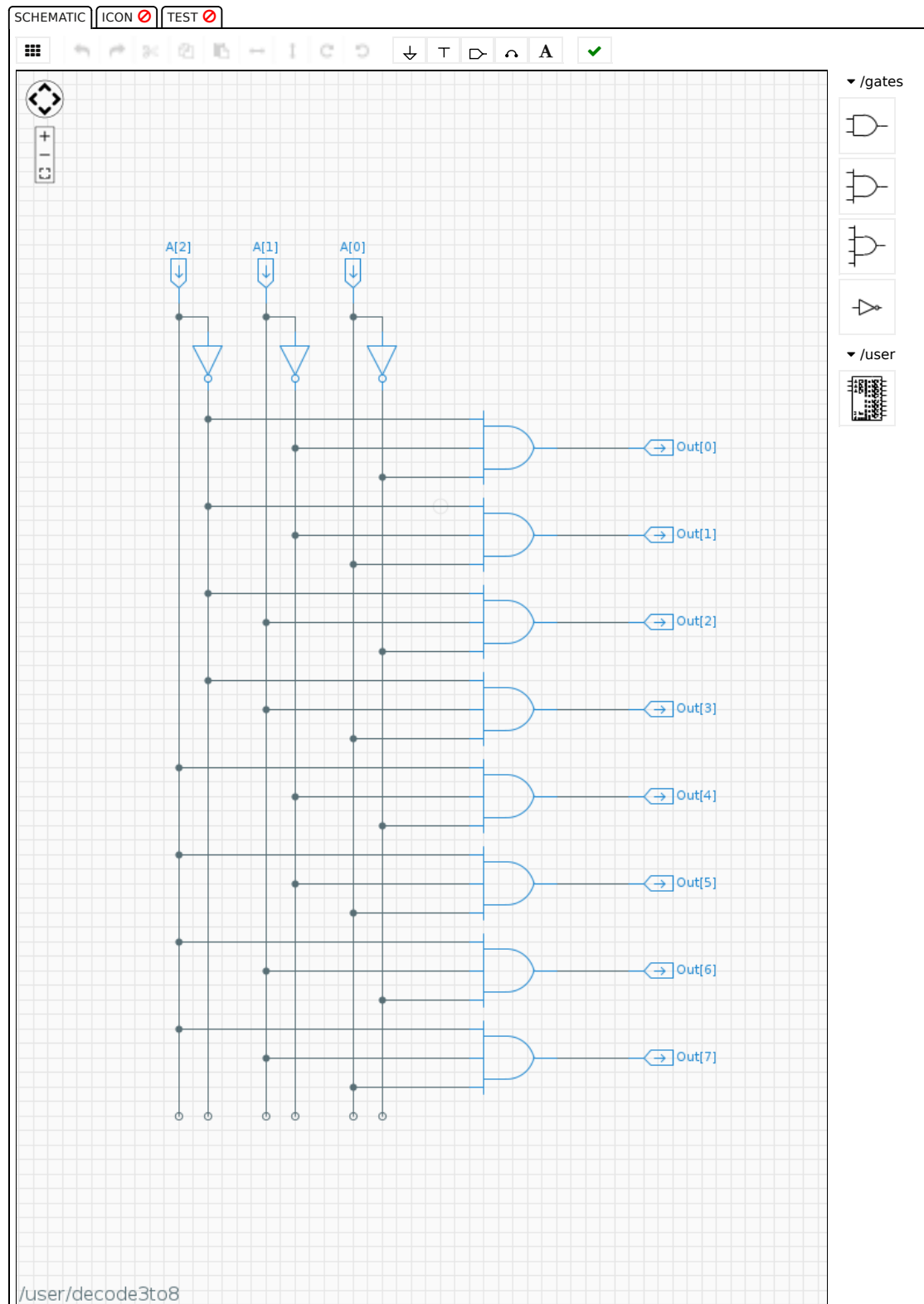

Click component to select, click and drag on background for area select, shift-click and drag on background to pan

[Jade 2.2.37 \(2015 © MIT EECS\)](#)

Check

Hide Answer

[Show Discussion](#)[New Post](#)

Help



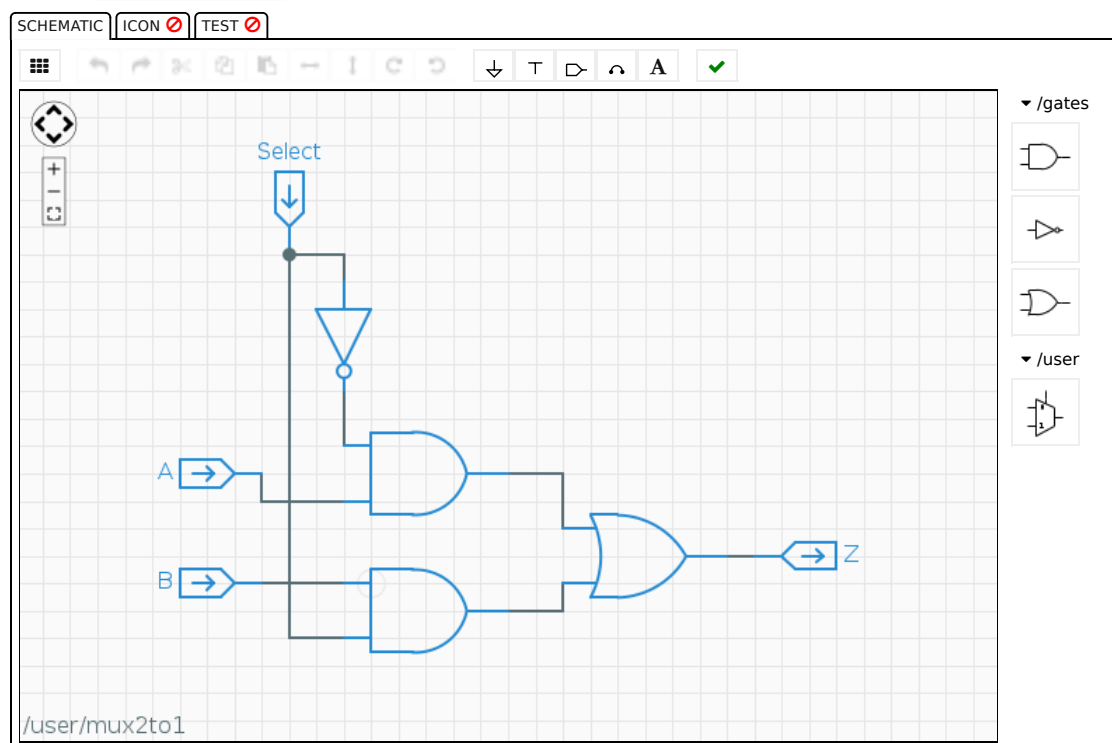

LAB 2. MUXES AND DECODERS

Design, using **NOT**, **AND**, and **OR** gates, a 1-bit 2-to-1 Mux and **test** it using the provided test file.

Treat A as the input which will be output to Z when Select is 0, and B as the input which will be output to Z when Select is 1.

After testing and checking, save this as a library component. You will need it for later labs!

2 TO 1 MULTIPLEXER (1/1 point)

Module:   

Click component to select, click and drag on background for area select, shift-click and drag on background to pan

[lade 2.2.37 \(2015 © MIT EECS\)](#)[Check](#)[Hide Answer](#)[Show Discussion](#)[New Post](#)

LAB 3. MUXES AND DECODERS

3 of 8

Design a 16-bit 2-to-1 Mux using **16** copies of your 1-bit library component and test it using the provided test file.

04/03/2015 03:21 PM

Treat A as the input which will be output to Z when Select is 0, and B as the input which will be output to Z when Select is 1.

You will need to load your previously designed "/user/mux2to1" component.


PLEASE NOTE: The 16-bit part we are designing now will show up in the /user/ parts area on the right. Make sure you are using the "/user/mux2to1" to build this lab! You can verify by checking the status text at the bottom of jade to see which part you are using.

After testing and checking, save this as a library component. You will need it for future labs!

Help

16-INPUT 2 TO 1 MULTIPLEXER (1/1 point)

Module: /user/mux2to1_16bit

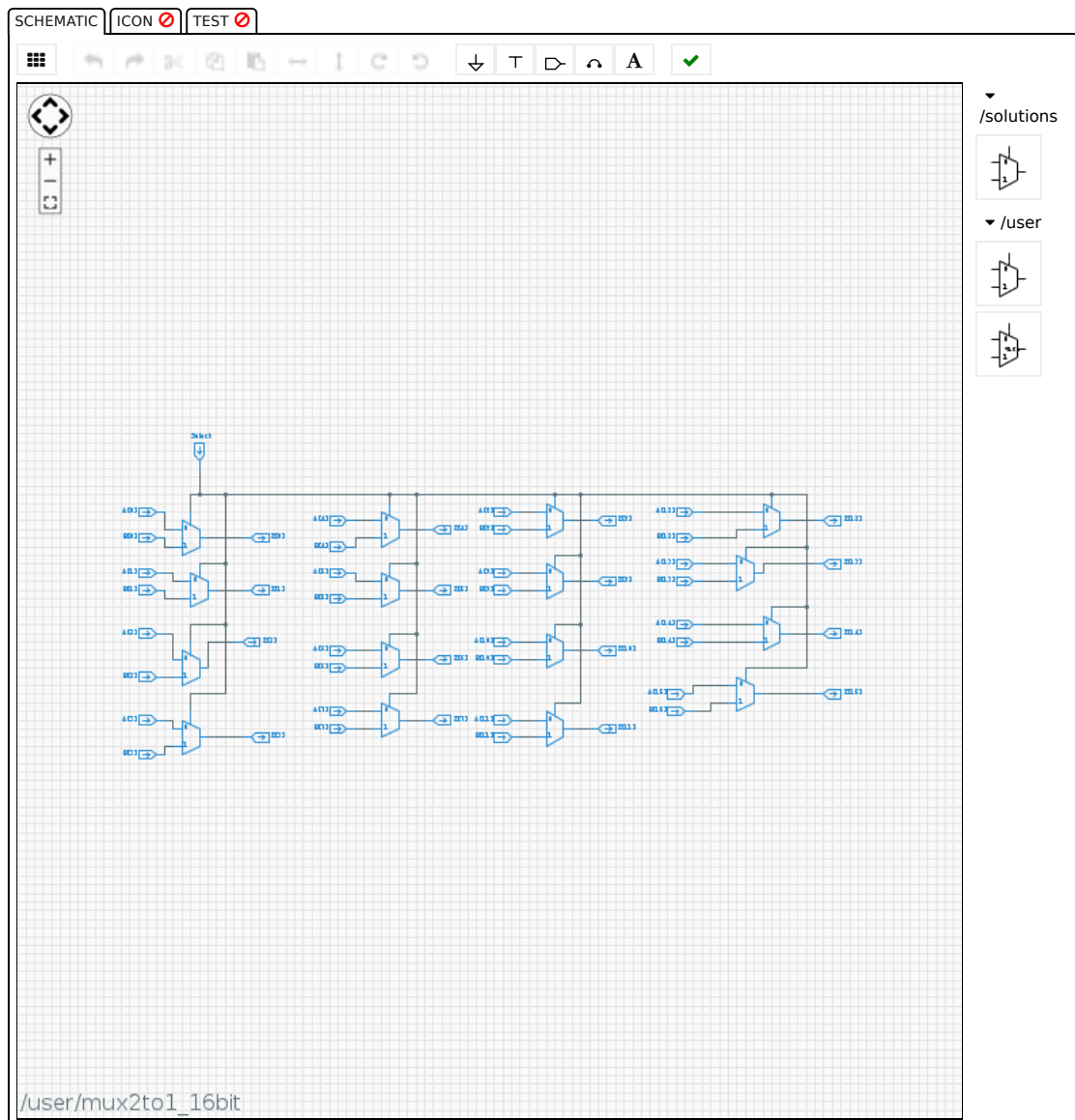

Click component to select, click and drag on background for area select, shift-click and drag on background to pan

[Jade 2.2.37 \(2015 © MIT EECS\)](#)

Check

Hide Answer

[Show Discussion](#)[New Post](#)

Help



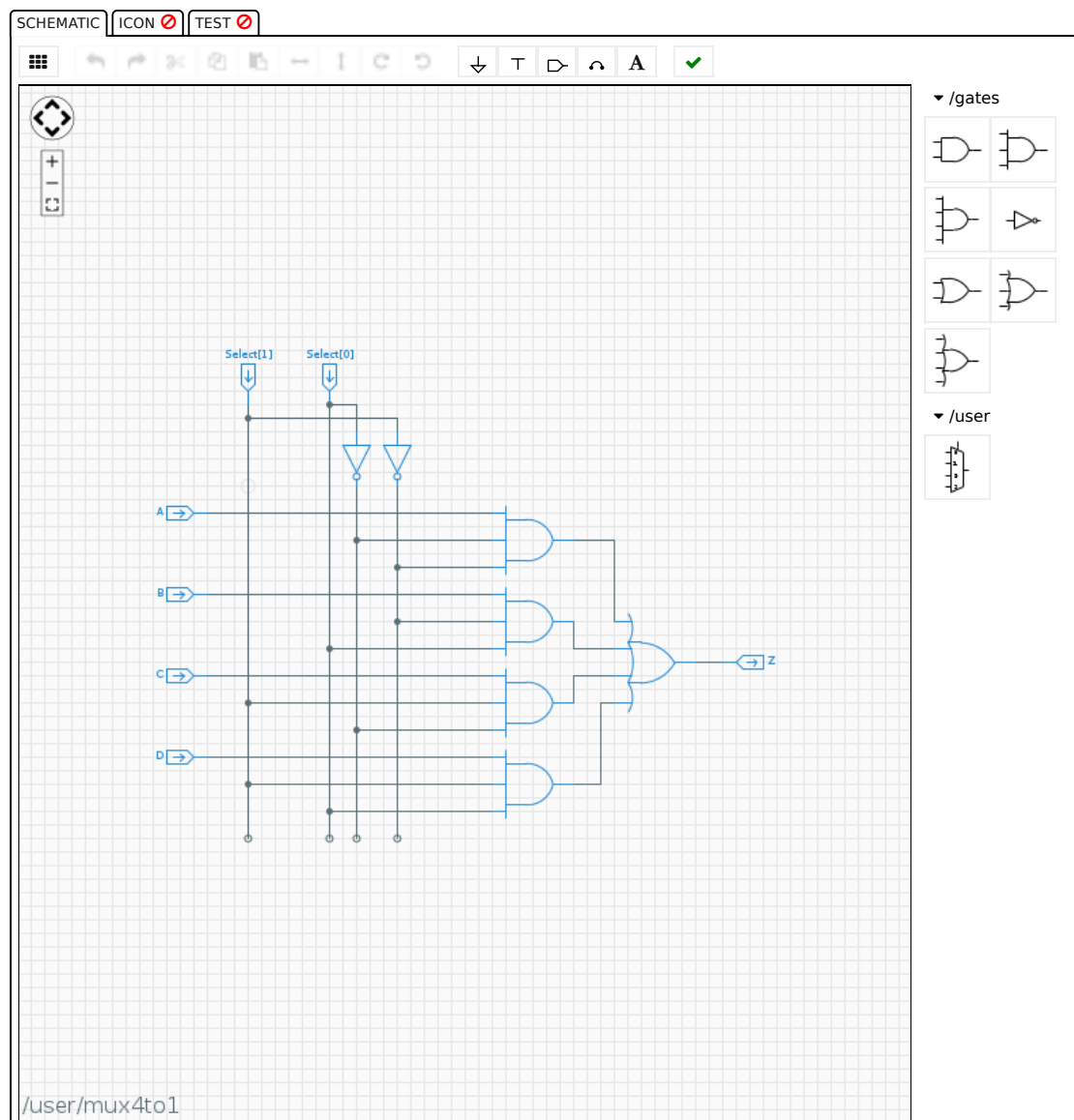

LAB 4. MUXES AND DECODERS

Design using **NOT**, **AND**, and **OR** gates a 1-bit 4-to-1 Mux and test it using the provided test file.

Treat A as the input to output to Z when Select[1:0] is 0, B when Select[1:0] is 1, C when Select[1:0] is 2, and D when Select[1:0] is 3.

After testing and checking, save this as a library component. You will want it for future labs!

4 TO 1 MULTIPLEXER (1/1 point)

Module:   

Click component to select, click and drag on background for area select, shift-click and drag on background to pan

[Jade 2.2.37 \(2015 © MIT EECS\)](#)

[Check](#)[Hide Answer](#)[Show Discussion](#)[New Post](#)

Help

LAB 5. MUXES AND DECODERS

Design a 16-bit 4-to-1 Mux using **16** copies of your 1-bit library component and test it using the provided test file.

Treat A as the input to output to Z when Select[1:0] is 0, B when Select[1:0] is 1, C when Select[1:0] is 2, and D when Select[1:0] is 3.

You will need to load your previously designed "/user/mux4to1" component.

PLEASE NOTE: The 16-bit part we are designing now will show up in the /user/ parts area on the right. Make sure you are using the "/user/mux4to1" to build this lab! You can verify by checking the status text at the bottom of jade to see which part you are using.

After testing and checking, save this as a library component.

16-INPUT 4 TO 1 MULTIPLEXER (1/1 point)

Module: /user/mux4to1_16bit


SCHEMATIC ☒ ICON ☒ TEST ☒

Help

/solutions



/user

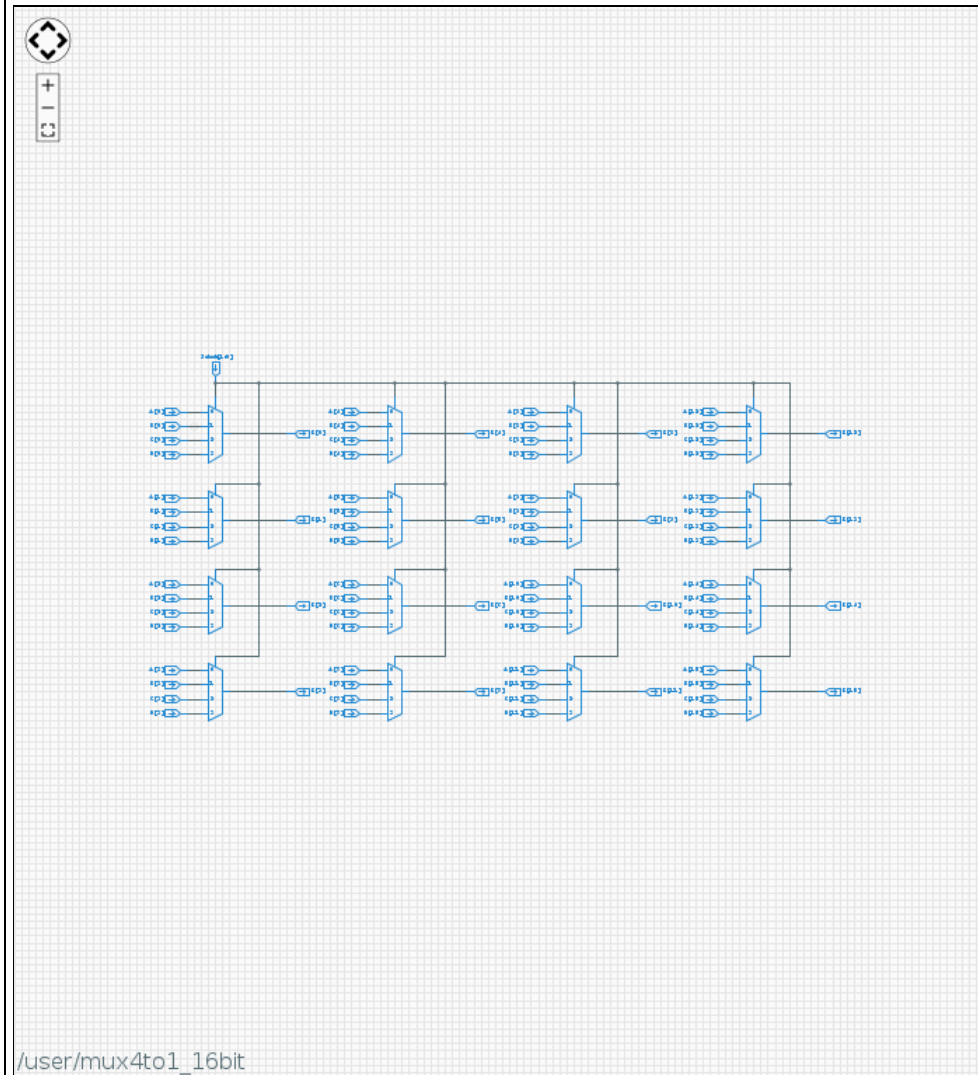

/user/mux4to1_16bit

Click component to select, click and drag on background for area select, shift-click and drag on background to pan.

[Jade 2.2.37 \(2015 © MIT EECS\)](#)

Check

Hide Answer

Show Discussion

New Post





universities. Online courses from MITx, HarvardX, MITx and Open edX are available. Typical

include biology, business, chemistry, computer science, economics, finance, electronics, engineering, food and nutrition, history, humanities, law, literature, math, medicine, music, philosophy, physics, science, statistics and more. EdX is a non-profit online initiative created by founding partners Harvard and MIT.

Help

© 2015 edX Inc.

EdX, Open edX, and the edX and Open edX logos are registered trademarks or trademarks of edX Inc.

[Terms of Service and Honor Code](#)

[Privacy Policy \(Revised 10/22/2014\)](#)



About edX

[About](#)

[News](#)

[Contact](#)

[FAQ](#)

[edX Blog](#)

[Donate to edX](#)

[Jobs at edX](#)

<https://courses.edx.org/courses/CornellX/ENGRI1210x/1...>

Follow Us



[Facebook](#)



[Twitter](#)



[LinkedIn](#)



[Google+](#)



[Tumblr](#)



[Meetup](#)



[Reddit](#)



[Youtube](#)