

Help

COMBINATIONAL V. SEQUENTIAL CIRCUITS

0:00 / 2:38

1.0x

Download transcript

.txt

Show Discussion

New Post


LATCHES

	6:55 / 6:57	1.0x			
--	-------------	------	--	--	--

[Download transcript](#) .txt[Show Discussion](#)[New Post](#)

1. CHECK YOUR UNDERSTANDING (1/1 point)

The RS inputs to an R-S latch are first 01, then 11, and then 10. Which of the following will be the output of Q (Please see resource above)?

- ☒ 0, then, 0, and then 1 
- ☐ 0, then, 1, and then 1
- ☐ 1, then, 0, and then 0
- ☐ 1, then, 1, and then 0

EXPLANATION

RS = 01 causes a reset operation, or an output of 0. RS = 11 retains the current output. RS = 10 causes a set operation, or an output of 1.

[Hide Answer](#)

You have used 2 of 2 submissions



EdX offers interactive online classes and MOOCs from the world's best universities. Online courses from MITx, HarvardX, BerkeleyX, UTx and many other universities. Topics include biology, business, chemistry, computer science, economics, finance, electronics, engineering, food and nutrition, history, humanities, law, literature, math, medicine, music, philosophy, physics, science, statistics and more. EdX is a non-profit online initiative created by founding partners Harvard and MIT.

© 2015 edX Inc.

EdX, Open edX, and the edX and Open edX logos are registered trademarks or trademarks of edX Inc.

[Terms of Service and Honor Code](#)

[Privacy Policy \(Revised 10/22/2014\)](#)



About edX

[About](#)

[News](#)

[Contact](#)


[FAQ](#)

[edX Blog](#)

[Donate to edX](#)


[Jobs at edX](#)


Follow Us


 [Facebook](#)


 [Twitter](#)


 [LinkedIn](#)

 [Google+](#)

 [Tumblr](#)

 [Meetup](#)

 [Reddit](#)

 [Youtube](#)