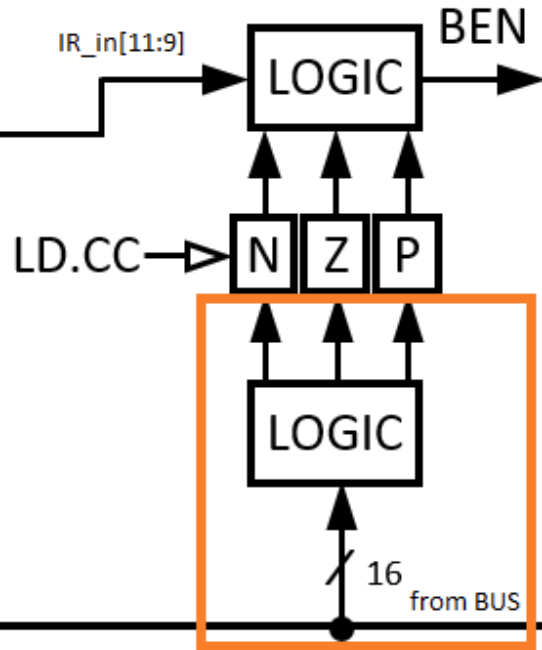


Help

Design the LC-3 Condition Code generation logic and test it using the provided test file.

The area of the LC-3 we are designing is shown here in the red box:



The input to this combinational logic circuit is a 16-bit two's complement value, and the outputs are N, Z, and P, only one of which should be a 1 for any given input value.

N is 1 when the input is a negative number, otherwise 0.

Z is 1 when the input is zero, otherwise it is 0.

P is 1 when the input is a positive number, otherwise it is 0.

Help

After testing and checking, save this as a library component. We will need it in future labs!

LC-3 LITE CONDITION CODE LOGIC (1/1 point)



[Check](#)[Hide Answer](#)[Show Discussion](#)[New Post](#)[Help](#)

EdX offers interactive online classes and MOOCs from the world's best universities. Online courses from MITx, HarvardX, BerkeleyX, UTx and many other universities. Topics include biology, business, chemistry, computer science, economics, finance, electronics, engineering, food and nutrition, history, humanities, law, literature, math, medicine, music, philosophy, physics, science, statistics and more. EdX is a non-profit online initiative created by founding partners Harvard and MIT.

© 2015 edX Inc.

4 of 5
EdX, Open edX, and the edX and Open edX logos are registered trademarks or trademarks of edX Inc.

About edX

[About](#)[News](#)[Contact](#)[FAQ](#)[edX Blog](#)[Donate to edX](#)[Jobs at edX](#)

Follow Us

[Facebook](#)[Twitter](#)[LinkedIn](#)[Google+](#)[Tumblr](#)[Meetup](#) 05/01/2015 02:50 PM



Reddit

<https://courses.edx.org/courses/CornellX/ENGRI1210x/1T2015/courseware/fae...>



Youtube

Help